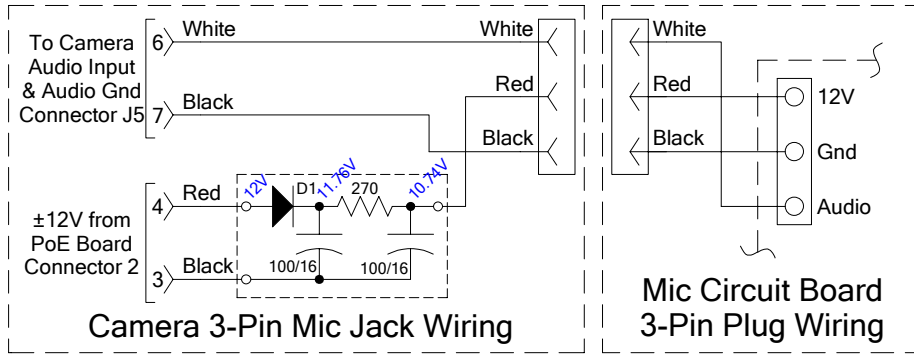



# Amplified Electret Mic Supply Voltage Filter

Dec 18 / 2015




Mic Circuit Supply Voltage Filter Board

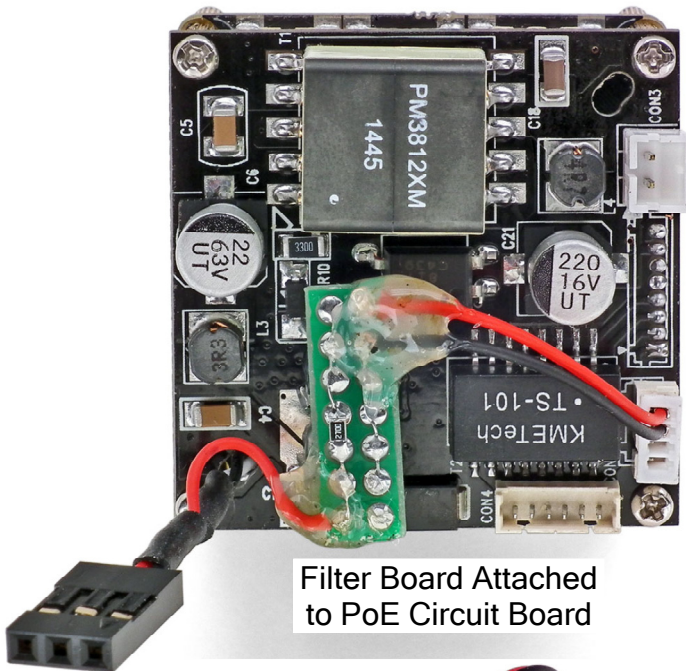\*\* Make D1 a Schottky diode to minimize the diode voltage drop.



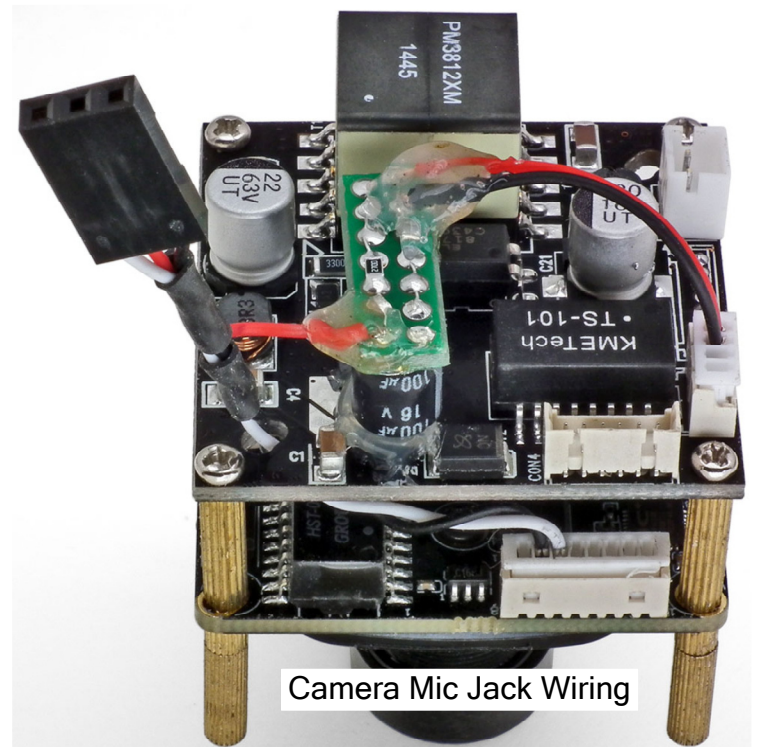Filter Board Attached to PoE Circuit Board



Camera Mic Jack Wiring

